

MULTIPLIERLESS FILTER DESIGN

Implementation of Digital Signal Processing

Sabih H. Gerez
University of Twente

MULTIPLIERLESS FILTER DESIGN

- Realization of filters without full-fledged multipliers
- Some slides based on support material by W. Wolf for his book *Modern VLSI Design, 3rd edition*. © W
- Partly based on following papers:
 - Hewlitt, R.M. and E.S. Swartzlander, "Canonical Signed Digit Representation for FIR Digital Filters", *IEEE Workshop on Signal Processing Systems, SiPS 2000*, Lafayette, LA, pp. 416-426, (2000).
 - Voronenko, Y. and M. Pueschel, *Multiplierless Multiple Constant Multiplication*, ACM Transactions on Algorithms, Vol. 3(2), (May 2007).
 - Aksoy, L., P. Flores and J. Monteiro, *A Tutorial on Multiplierless Design of FIR Filters: Algorithms and Architectures*, Circuits, Systems and Signal Processing, Vol.33(6), pp. 1689-1719, (2014).

TOPICS


- Multiplier wrap-up:
 - Array multiplier
 - Booth multiplier
- Filter structures: direct, transposed and hybrid forms
- Canonical signed digit
- Optimal single and multiple-constant multiplication
- Choosing coefficients

MULTIPLICATION

- Distinguish between:
 - Multiplication of two variables
 - Multiplication of one variable by a constant (*scaling*)
⇒ opportunities of optimization
- Constants:
 - Can be considered as given
 - Can be specially chosen
- Implementation:
 - One-to-one
 - Resource sharing
 - In software, on processor without hardware multiplier
[How does that work?]

ELEMENTARY SCHOOL ALGORITHM


Unsigned numbers!

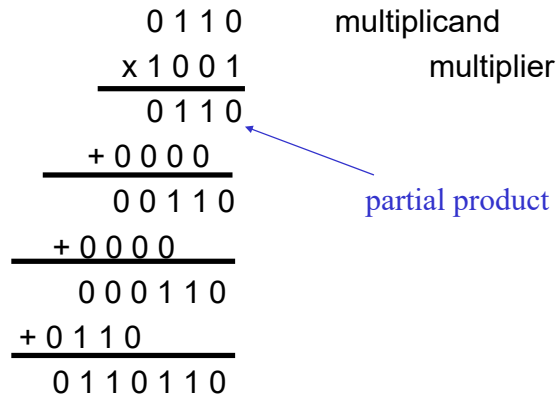


ARRAY MULTIPLIER

- Array multiplier is an efficient layout of a combinational (parallel-parallel) multiplier.
- Array multipliers may be pipelined to decrease clock period at the expense of latency.

ARRAY MULTIPLIER ORGANIZATION

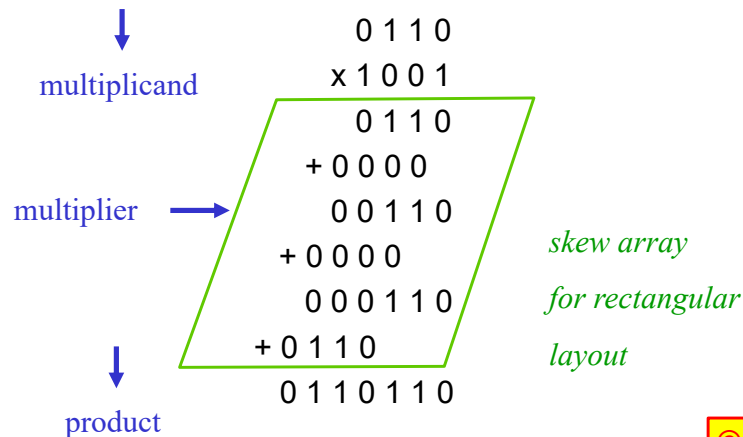


UNSIGNED 4X4 ARRAY MULTIPLIER

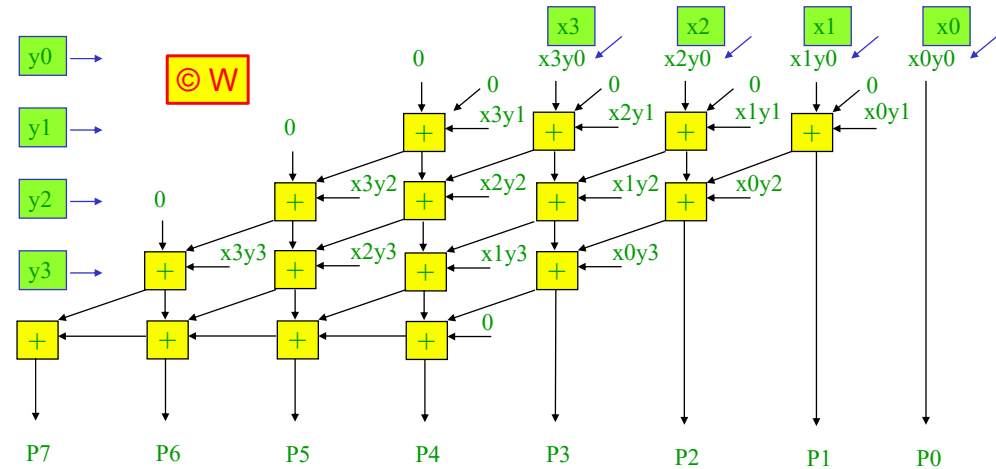

ARRAY MULTIPLIER COMPONENTS

- AND gates
- FULL ADDERS
- HALF ADDERS

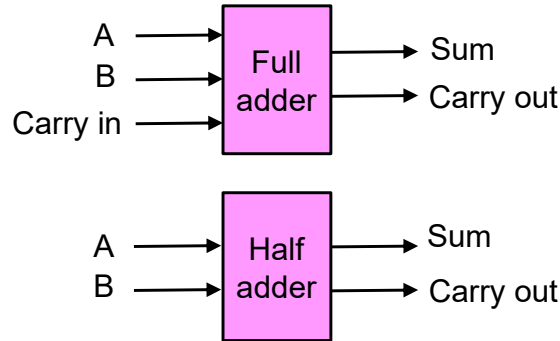

- Fast multiplication amounts to reducing the critical path.
- [What is the main issue when doing signed multiplications?]

2'S COMPLEMENT MULTIPLICATION (1)

- An n-bit number X, and an m-bit number Y:

$$X = -x_{n-1}2^{n-1} + \sum_{i=0}^{n-2} x_i 2^i$$

$$Y = -y_{m-1}2^{m-1} + \sum_{i=0}^{m-2} y_i 2^i$$

2'S COMPLEMENT MULTIPLICATION (2)

- Product:

$$P = XY = x_{n-1}y_{m-1}2^{m+n-2} + \sum_{i=0}^{n-2} \sum_{j=0}^{m-2} x_i y_j 2^{i+j} + -2^{n-1} \sum_{i=0}^{m-2} y_i x_{n-1} 2^i - 2^{m-1} \sum_{i=0}^{n-2} x_i y_{m-1} 2^i$$

2'S COMPLEMENT MULTIPLICATION (3)

- Note that: $-x \cdot 2^n = -2^n + \bar{x} \cdot 2^n$
- and: $\sum_{i=0}^k -2^i = 1 - 2^{k+1}$
- Therefore:

$$\begin{aligned} -2^{n-1} \sum_{i=0}^{m-2} y_i x_{n-1} 2^i &= 2^{n-1} \sum_{i=0}^{m-2} -2^i + 2^{n-1} \sum_{i=0}^{m-2} \overline{y_i x_{n-1}} 2^i \\ &= -2^{n+m-2} + 2^{n-1} + 2^{n-1} \sum_{i=0}^{m-2} \overline{y_i x_{n-1}} 2^i \end{aligned}$$

2'S COMPLEMENT MULTIPLICATION (4)


- The product becomes:

$$P = XY = x_{n-1}y_{m-1}2^{n+m-2} + \sum_{i=0}^{n-2} \sum_{j=0}^{m-2} x_i y_j 2^{i+j} - 2^{n+m-1} + 2^{n-2} + 2^{m-2} + 2^{n-1} \sum_{i=0}^{m-2} y_i x_{n-1} 2^i + 2^{m-1} \sum_{i=0}^{n-2} x_i y_{m-1} 2^i$$

BAUGH-WOOLEY MULTIPLIER

- Algorithm for two's-complement multiplication.
- Careful processing of partial products leads to:
 - Array with only additions, no subtractions
 - No hardware for sign extensions in upper left corner
- Achieved by:
 - Negation of some partial products
 - Injection of ones in some array positions

BAUGH-WOOLEY SIGNED 4X4 ARRAY MULTIPLIER

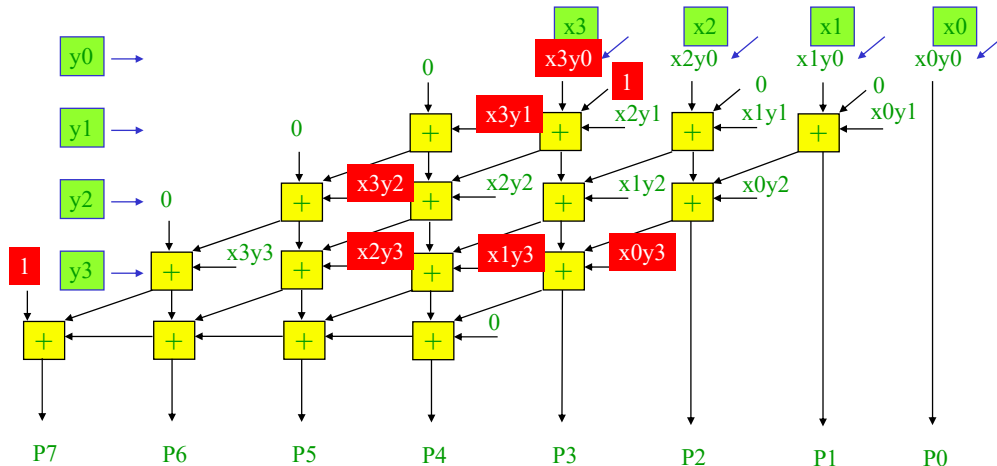

BOOTH MULTIPLIER

- Encoding scheme to reduce number of stages in multiplication.
- Performs two bits of multiplication at once; requires half the stages.
- Each stage is slightly more complex than an adder.

BOOTH ENCODING

- The wanted product: $x \cdot y$.
- Two's-complement form of multiplier:

$$y = -2^n y_n + 2^{n-1} y_{n-1} + 2^{n-2} y_{n-2} + \dots$$
- Rewrite using $2^a = 2^{a+1} - 2^a$:

$$y = 2^n (y_{n-1} - y_n) + 2^{n-1} (y_{n-2} - y_{n-1}) + 2^{n-2} (y_{n-3} - y_{n-2}) + 2^{n-3} (y_{n-4} - y_{n-3}) + \dots$$

$$y = 2^{n-1} (2(y_{n-1} - y_n) + (y_{n-2} - y_{n-1})) + 2^{n-3} (2(y_{n-3} - y_{n-2}) + (y_{n-4} - y_{n-3})) + \dots$$

Taking steps of 2
- Consider first two terms: by looking at three bits of y , we can determine whether to add x , $2x$, $-x$, $-2x$, or 0 to partial product.

BOOTH ACTIONS


y_i	y_{i-1}	y_{i-2}	increment $(2(y_{i-1} - y_i) + y_{i-2} - y_{i-1})$
0	0	0	0x
0	0	1	1x
0	1	0	1x
0	1	1	2x
1	0	0	-2x
1	0	1	-1x
1	1	0	-1x
1	1	1	0x



BOOTH EXAMPLE

- $x = 011001$ (25_{10}), $y = 101110$ (-18_{10}).
 - $y_1 y_0 y_{-1} = 100$, $P_1 = P_0 - (10 \cdot 011001) = 11111001110$. $-2 \cdot 1 \cdot x$
 - $y_3 y_2 y_1 = 111$, $P_2 = P_1 + 0 = 11111001110$. $0 \cdot 4 \cdot x$
 - $y_5 y_4 y_3 = 101$, $P_3 = P_2 - 0110010000 = 11000111110$ (-450_{10}).
- (bitwise invert 25) 100110
+1
(-25) 100111
(-50) 1001110
- 1 · 16 · x

BOOTH STRUCTURE

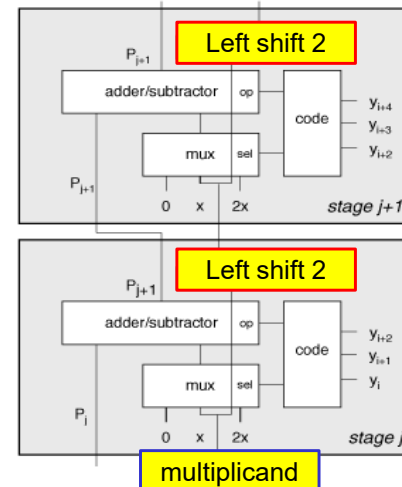

Comparison with array multiplier:

- Depth for partial product generation is half, which should result in faster and smaller solution [not always].
- Some extra overhead for Booth encoding, etc.




FIR-FILTER DIRECT FORM (1)

- FIR = *finite impulse response*
- Difference equation:


$$y[n] = \sum_{k=0}^N b_k \cdot x[n - k]$$

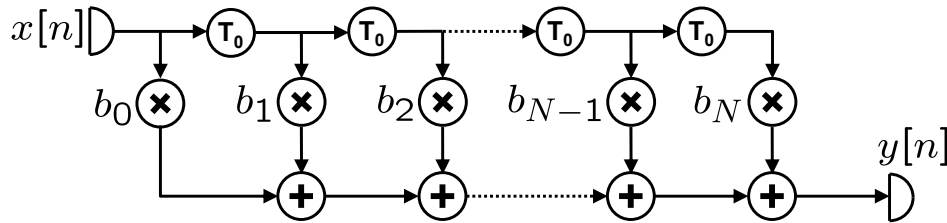- Where is the critical path?
- How long is it as function of N ?



FIR-FILTER DIRECT FORM (2)

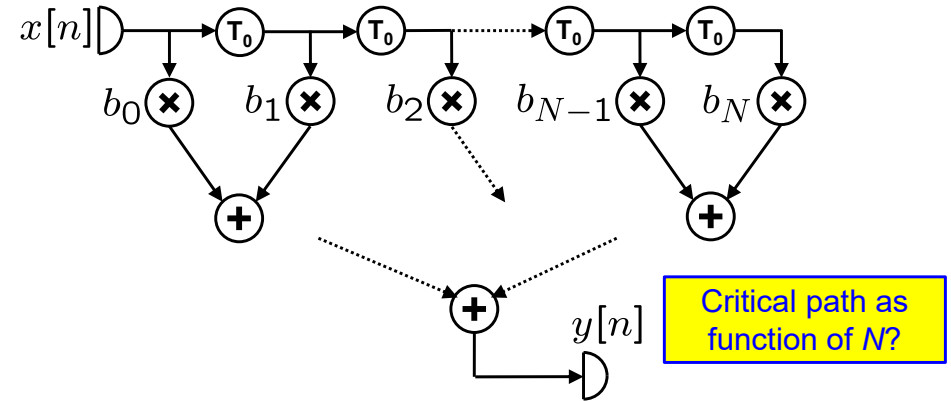
- Use a binary tree structure for the additions:



- Critical path as function of N ?


CLASSICAL RETIMING

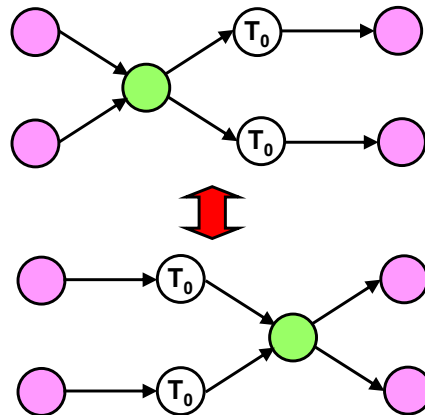- It is allowed to “push delay elements” through a computation:
 - From inputs to outputs or
 - From outputs to inputs
- Compute-and-then-delay is the same as delay-and-then-compute.
- Allowed in cyclic DFGs.




CUT-SET RETIMING

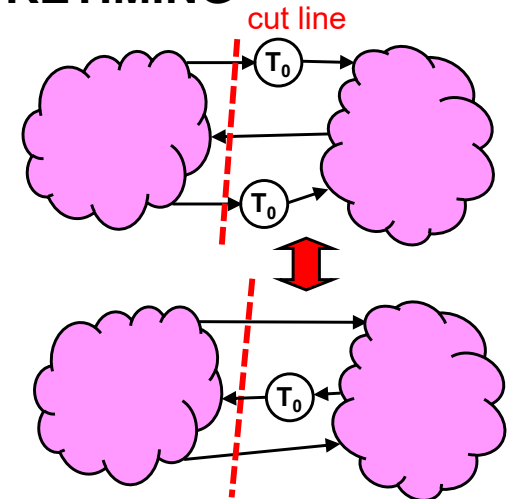
- Generalization of classical retiming.
- Cut-set** = set of edges that cuts a graph in two when removed.
- Given a cut-set of any DFG, the DFG’s behavior remains unchanged if the same number of delays are added (removed) on incoming edges as are removed (added) on outgoing edges.




FIR-FILTER DIRECT FORM (3)

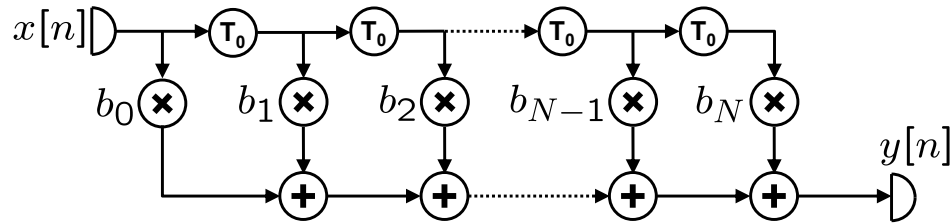

- Reverse order of additions:

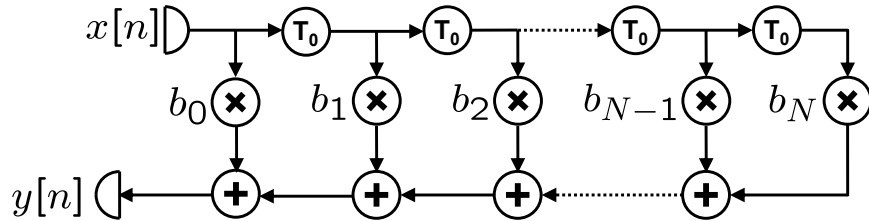


CUT-SET RETIMED FIR-FILTER

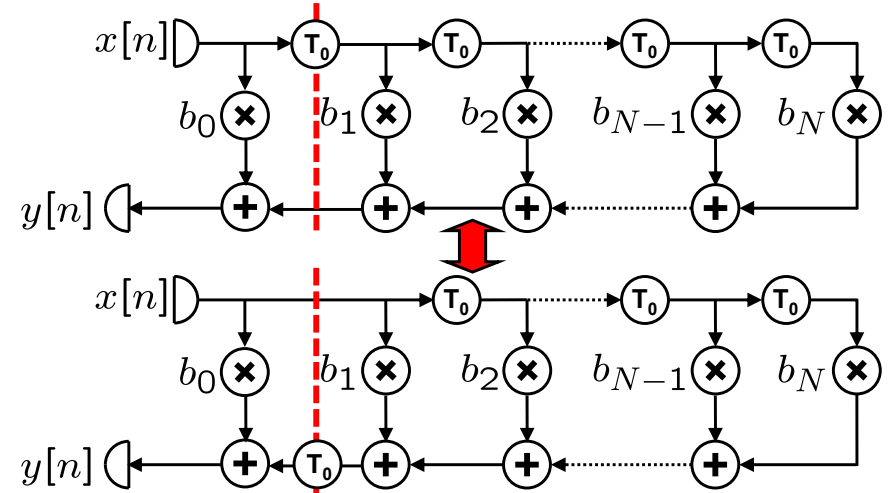

FIR-FILTER TRANSPOSED FORM

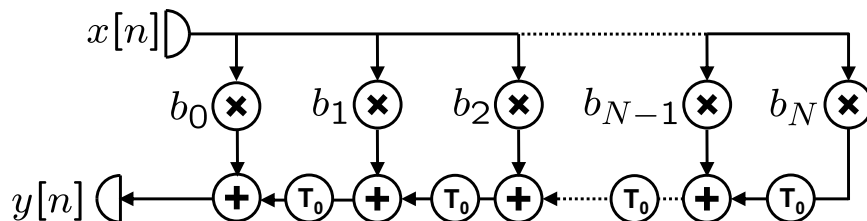- Computationally equivalent to direct form
- Can be obtained by systematically applying cut-set retiming.
- Now, all multiplications share one input



FIR FILTER HYBRID FORM


- The direct-form-implementation has all its delays in the input line.
- The transposed-form implementation has all delays on the output line.
- Hybrid-form implementation has part of the delays in the input line and part on the output line. See paper by Aksoy et al. for more details.

IIR FILTER


- IIR = *infinite impulse response*
- Difference equation:

$$y[n] = \sum_{k=1}^N a_k \cdot y[n - k] + \sum_{k=0}^N b_k \cdot x[n - k]$$

IIR-FILTER DIRECT FORM 1

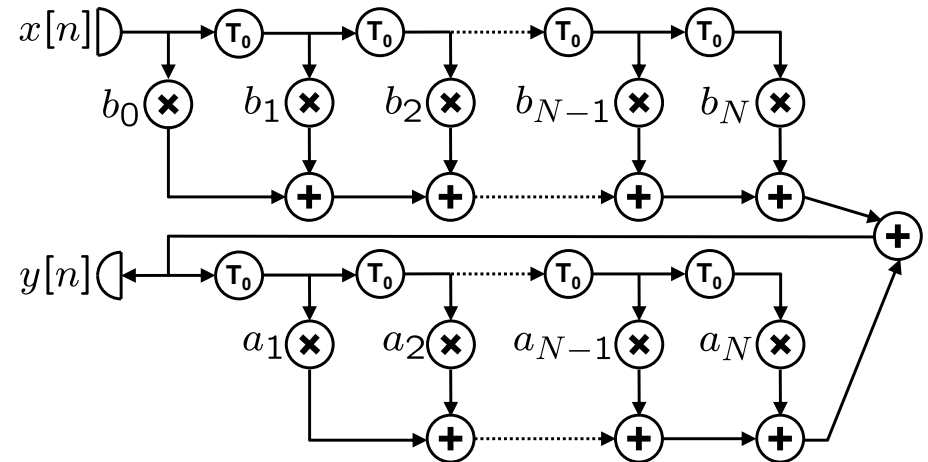

IIR-FILTER TRANSPOSED FORM

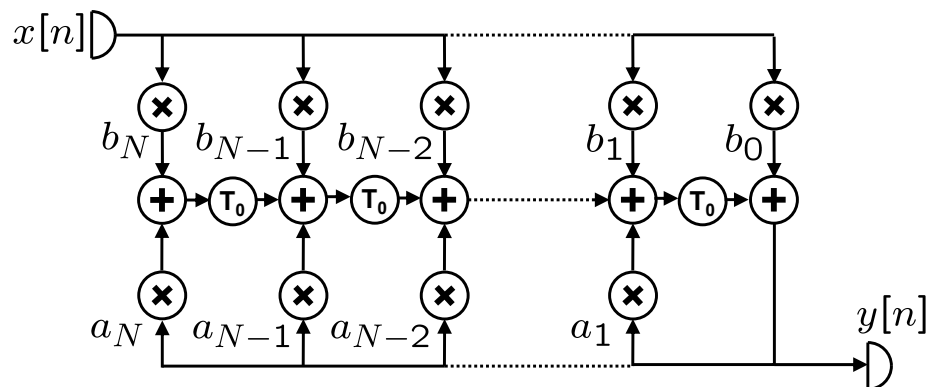

SCALING: BOUNDS ON ADDITIONS (1)

- Consider multiplication of x by $71 = 1000111_2$.
- Additions-only solution:

$$71x = (x \ll 6) + (x \ll 2) + (x \ll 1) + x$$
 (realized by means of 3 shifts and 3 additions; shifts by a constant costs only wires in hardware)
- Subtractions-only solution:

$$71x = ((x \ll 7) - x) - (x \ll 5) - (x \ll 4) - (x \ll 3)$$
 (realized by means of 4 shifts and 4 subtractions)

SCALING: BOUNDS ON ADDITIONS (2)

- In general, if b is the number of bits, z the number of zeros and o the number of ones ($b = z + o$):
 - The additions-only solution requires $o - 1$ additions.
 - The subtractions-only solution requires $z + 1$ subtractions.
- There is always a solution with at most $b/2 + O(1)$ additions or subtractions (just take the cheapest of the two solutions).
- The *average* cost is also $b/2 + O(1)$.
- Booth encoding has also the same cost.
- Can it be done better?

SIGNED POWER-OF-TWO REPRESENTATION

- Uses three-valued digits instead of binary digits: $0, 1, \bar{1}$
- A 1 at position k means a contribution of 2^k to the final value (as usual).
- A $\bar{1}$ at position k means a contribution of -2^k to the final value.
- Example: $101\bar{1}00\bar{1} = 64 + 16 - 8 - 1 = 71$

CANONICAL SIGNED-DIGIT (CSD)

- Special case of signed-digit power-of-two, with minimal number of non-zero digits.
- Canonical = unique encoding.
- When used to minimize additions in constant multiplication, reduces number of operations to $b/3 + O(1)$ in average, but still $b/2 + O(1)$ in worst case.
- Example: $100100\bar{1} = 64 + 8 - 1 = 71$

TWO'S COMPLEMENT TO CSD CONVERSION (1)

- Two's complement number: $X = x_{n-1}x_{n-2} \dots x_1x_0$
- Target: $C = c_{n-1}c_{n-2} \dots c_1c_0$
- Start from LSB and proceed to MSB using table on next slide
- Dummy value (sign extension): $x_n = x_{n-1}$
- Carry-in, initialized to 0.

2'S COMPLEMENT TO CSD CONVERSION (2)

carry-in	x_{i+1}	x_i	carry-out	c_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	-1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	-1
1	1	1	1	0

Hewlett & Swartzlander, Table 2


CSD NOT OPTIMAL

- CSD has minimal number of non-zeros, but is still not optimal for the "single constant multiplication" problem.
- How come?

SINGLE-CONSTANT MULTIPLICATION

- Number of operations can be reduced by allowing shifting and adding intermediate results
- Example, goal is to multiply by $45 = 101101_2 = 10\bar{1}0\bar{1}01$

Voronenko & Pueschel, Figure 2

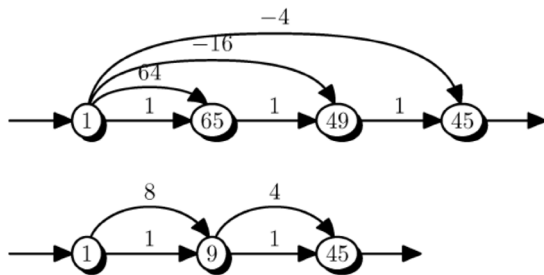

3x add/sub

$$65x = x + 64x$$

$$49x = 65x - 16x$$

$$45x = 49x - 4x$$

2x add/sub


$$9x = 8x + x$$

$$45x = 5(9x) = 9x + 4(9x)$$

MULTIPLE-CONSTANT MULTIPLICATION

- Even more opportunities for optimization occur when multiple constants can be optimized at the same time (think of the transposed form of a FIR filter).
- Example:

Voronenko & Pueschel, Figure 5

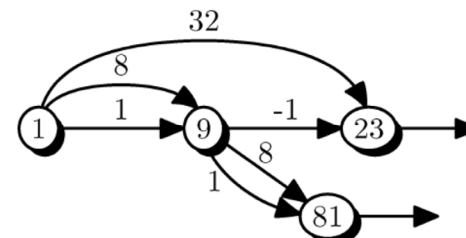

$$9x = 8x + x$$

$$23x = 32x - 9x$$


$$81x = 8(9x) + 9x$$

COMPUTATIONAL COMPLEXITY

- The optimization of the implementation for both the single-constant and multiple-constant multiplication problems is NP-complete.
- Powerful heuristics are available.
- Try SPIRAL on-line application:

<http://spiral.ece.cmu.edu/mcm/gen.html>

CONSTANT MATRIX-VECTOR MULT. (1)

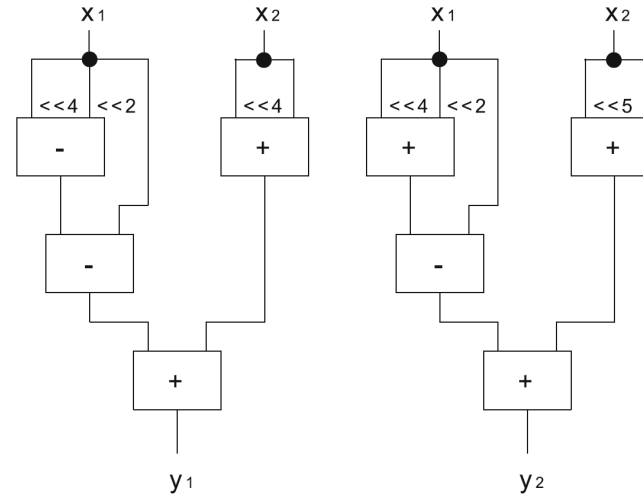

Applications in hybrid implementations of FIR filters


$$y_1 = 11 \cdot x_1 + 17 \cdot x_2$$

$$y_2 = 19 \cdot x_1 + 33 \cdot x_2$$

Unoptimized:
8 add/sub

Aksoy et al.,
Figure 3

CONSTANT MATRIX-VECTOR MULT. (2)

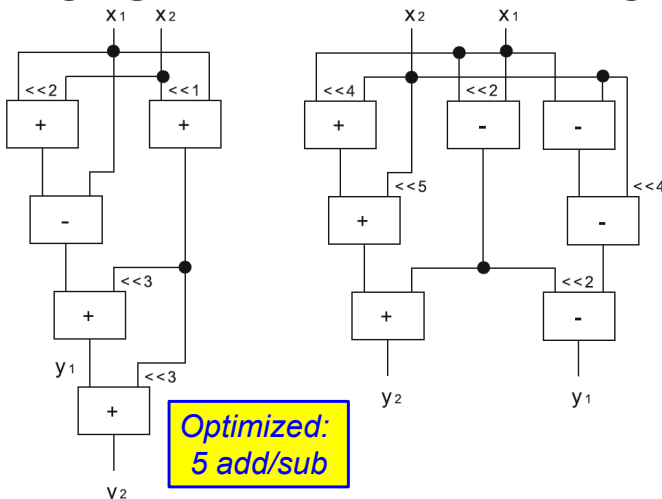

Optimized with depth constraint of 3:
7 add/sub

Optimized:
5 add/sub

Aksoy et al.,
Figure 5

CHOOSING THE COEFFICIENTS

- Until now, the discussion was about implementing filters with given constant coefficients as efficiently as possible.
- Classical approach starts from floating-point coefficients as e.g. computed in Matlab and a “blind” fixed-point conversion.
- It is even more interesting to take cheap implementation as a criterion during filter design. A problem description could e.g. be:
 - Given a number T , construct a filter with at most T non-zero bits in its set of coefficients while at the same time satisfying the usual criteria such as “bandwidth”, “pass band ripple”, etc.