

SYSTEM-ON-CHIP DESIGN

LOGIC SYNTHESIS WITH STANDARD CELLS

OUTLINE


- Register-transfer level design
- Edge-triggered flipflops
- Standard cells
- Delay
- Logic optimization
- Clock skew and clock trees

Note: some of the slide material for this presentation has been taken from the slides belonging to:

Wolf, W., *Modern VLSI Design, System-on-Chip Design*, Third Edition, Prentice Hall PTR, Upper Saddle River, New Jersey, (2002).

REGISTER-TRANSFER LEVEL (1)

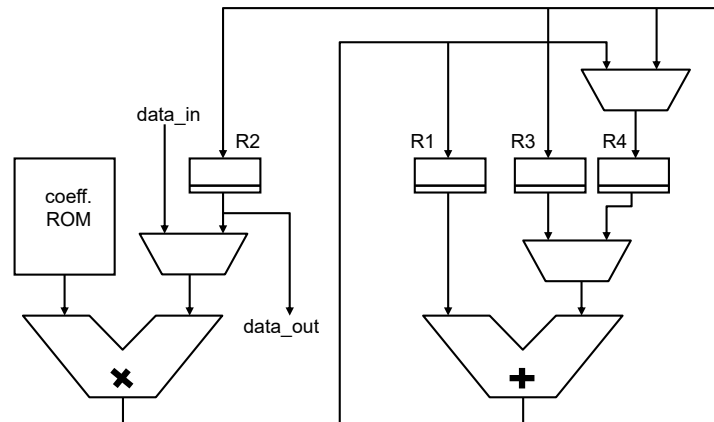
- *Register-transfer level (RTL): the most common abstraction level encountered in digital design*




REGISTER-TRANSFER LEVEL (2)

- Signals start either in a register or a *primary input*.
- Signals end either in a register or a *primary output*.
- Registers change their value at the rising edge of the clock (implemented by positive edge-triggered flipflops).
- Signals have time to propagate through *combinational logic* until next rising edge of clock.
- Hardware behaves as a *finite state machine (FSM)*, where the registers hold the *current state* and the combinational logic computes the *next state*.

FSM STRUCTURE (MEALY)

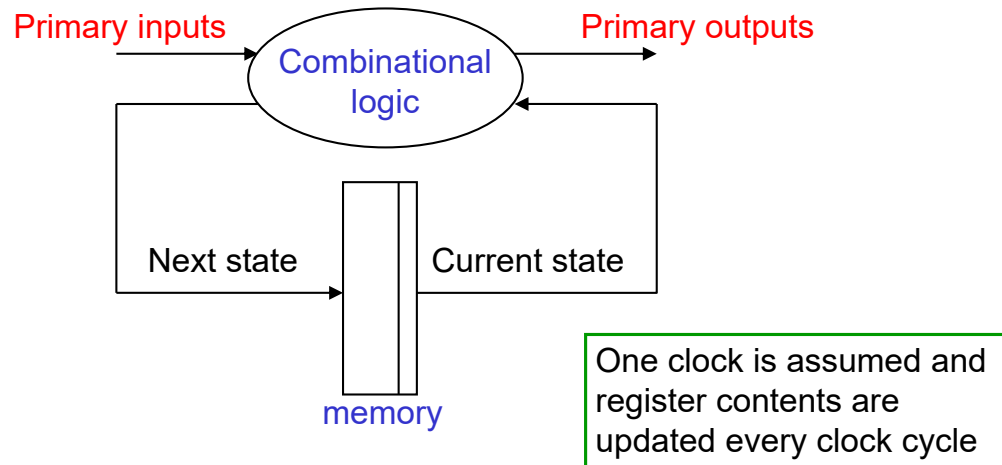


FSM STRUCTURE (MOORE)

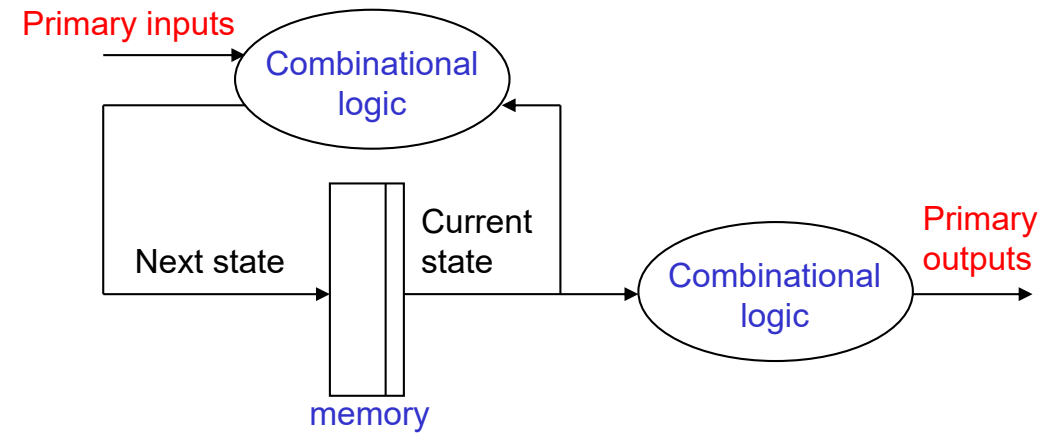

EDGE-TRIGGERED FLIP-FLOP

- The *edge-triggered flip-flop* is the most frequently used memory logic in sequential circuitry.
- It requires the data only to be stable within the setup and hold margins.
- One has a robust design style when an entire circuit exclusively uses positive (or negative) edge-triggered flip-flops.

POSITIVE EDGE-TRIGGERED FLIP-FLOP

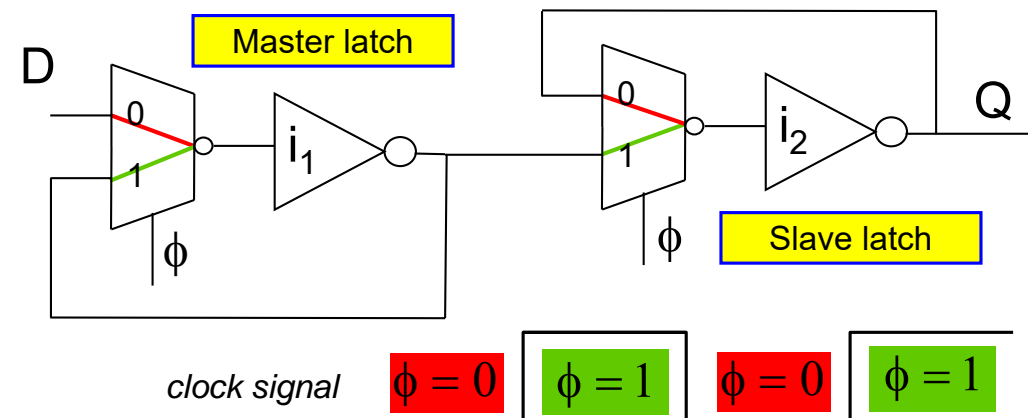

Only the input value at the rising clock transition is captured!

MASTER-SLAVE OPERATION

- $\Phi = 0$: master latch output follows input D; slave latch keeps its value.
- Rising edge of Φ : value of D now propagates to slave's output.
- $\Phi = 1$: master latch keeps its value; slave latch is transparent and follows master.

STANDARD-CELL-BASED DESIGN (1)

- The designer is given a *library* of elementary circuits called *cells*.
- The design of library cells (from transistors) is a specialized task and is done by a dedicated group or company.
- Library information consists of:
 - cell function and simulation models (delays!)
 - cell layouts.


STANDARD-CELL-BASED DESIGN (2)

- Designing amounts to delivering a *netlist* of cells for layout.
- The netlist is generally obtained by means of *logic synthesis*.
- The netlist is mapped on a layout by means of *placement* and *routing*.

STANDARD-CELL LAYOUT (1)

- Cells use a limited number of metal layers.
- Power wires run horizontally through the cells using the same pitch; horizontal cell *abutment* can be applied.
- Other wires have *terminals* on the top and/or bottom of the cell; wiring channels realize the interconnection of terminals according to netlist.


STANDARD-CELL LAYOUT (2)

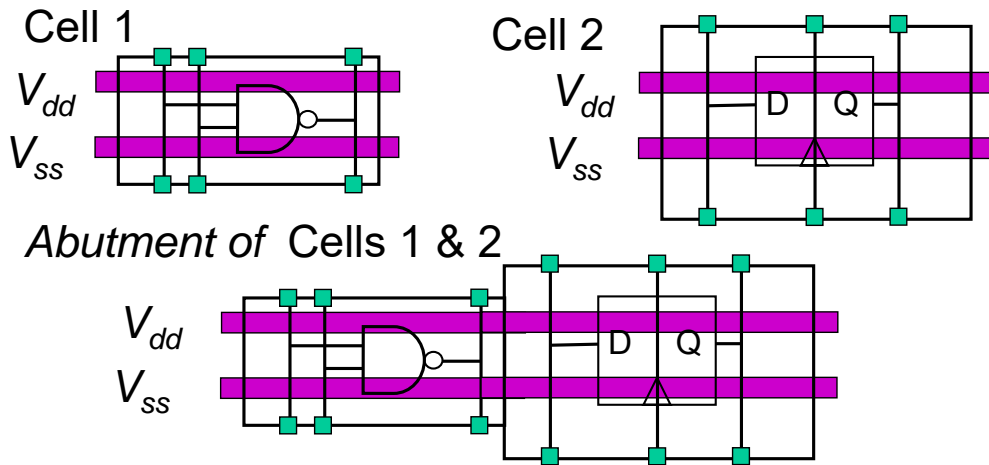

STANDARD-CELL LAYOUT (3)


- Cells are organized in multiple rows with wiring channels in between.
- Routing can use metal layers on top of cells.
- An entire chip will in general consist of multiple blocks of standard cells, as well as memories, data paths, etc.
- Place-and-route software is used fit the standard cells inside the area delimited by large blocks such as memories.

STANDARD-CELL LAYOUT (4)

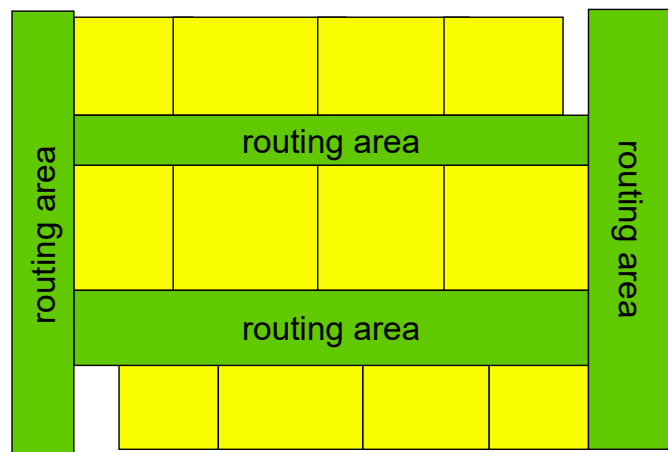

DELAY


- Assume ideal input (step), RC load.

 

PROPAGATION DELAY RISE/FALL TIMES (1)

- *Propagation delay* is measured between the 50% transition moment of input and the 50% transition of output; it is the average of *high-to-low* and *low-to-high* delays.
- *Rise time* is measured from the 10% to the 90% points in the output transition.
- *Fall time* is the reverse (from 90% to 10%).

PROPAGATION DELAY RISE/FALL TIMES (2)

 

DRIVING LARGE LOADS


- Sometimes, large loads must be driven:
 - off-chip;
 - long wires on-chip.
- Sizing up the driver transistors only pushes back the problem—driver now presents larger capacitance to earlier stage.

- The standard-cell library has cells AND2D1, AND2D2, AND2D4:
 - What is the difference between the cells?

OPTIMAL SIZING


- Use a chain of inverters, each stage has transistors larger than previous stage.
- Optimal number of stages $n_{opt} = \ln(C_{big}/C_g)$.
- Driver sizes are exponentially tapered.

CASCADED DRIVER CIRCUIT

 


PATH DELAY

 - In combinational logic signals need to pass a sequence of gates, each contributing some amount of delay.




SIGNALS IN FLIP-FLOP SYSTEM

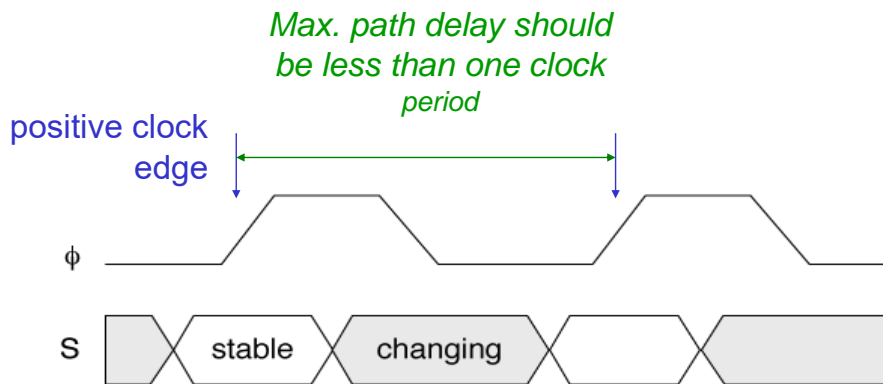


CRITICAL PATH

 - Critical path** = path which creates longest delay




LOGIC REWRITES

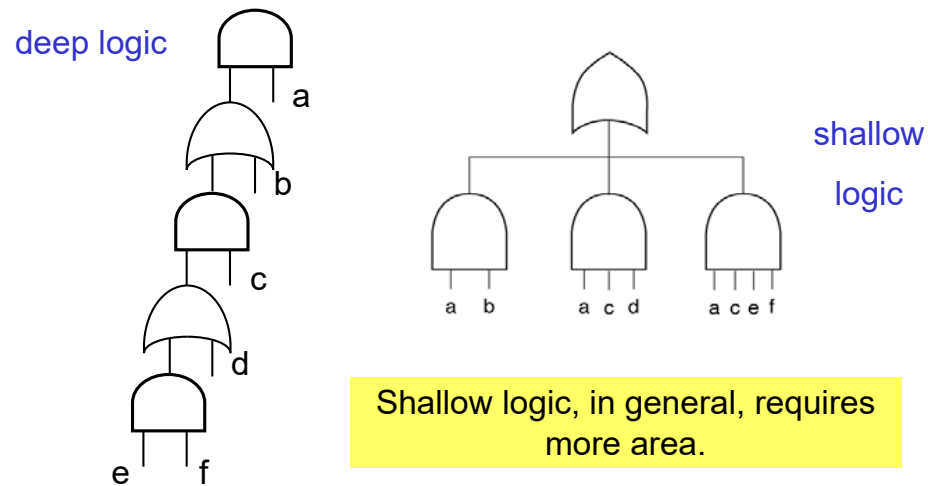

© Sabih H. Gerez, University of Twente, The Netherlands

TIME-AREA TRADE-OFF IN LOGIC SYNTHESIS

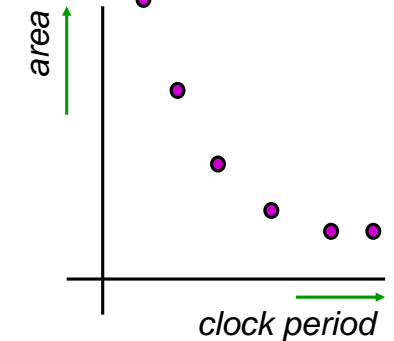- In general, one can make a circuit faster by using more area.
- Example: a *carry-ripple adder* is small but relatively slow; a *carry-lookahead adder* is faster, but larger.
- In logic synthesis one constrains the clock period and the synthesis tool will choose the implementation that fits the constraint.



© Sabih H. Gerez, University of Twente, The Netherlands

LOGIC OPTIMIZATION

- Logic synthesis programs transform Boolean expressions into logic gate networks in a particular library.
- Optimization goals: minimize area, meet delay constraint.

© Sabih H. Gerez, University of Twente, The Netherlands

TECHNOLOGY-INDEPENDENT OPTIMIZATIONS

- Works on Boolean expression equivalent.
- Estimates size based on number of literals.
- Uses factorization, resubstitution, minimization, etc. to optimize logic.
- Technology-independent phase uses simple delay models.

© Sabih H. Gerez, University of Twente, The Netherlands

TECHNOLOGY-DEPENDENT OPTIMIZATIONS


- Maps Boolean expressions into a particular cell library.
- Mapping may take area and delay into account.
- May perform some optimizations in addition to simple mapping.
- Allows more accurate delay models.
- In state-of-the-art design, technology-dependent optimization continues during layout (placement and routing):
 - Think of buffering to compensate for parasitic delays.

CLOCK TERMINOLOGY

- *Clock edge*: rising or falling transition.
- *Duty cycle*: fraction of clock period for which clock is active (e.g., for active-low clock, fraction of time that clock is 0).


MEMORY-ELEMENT PARAMETERS

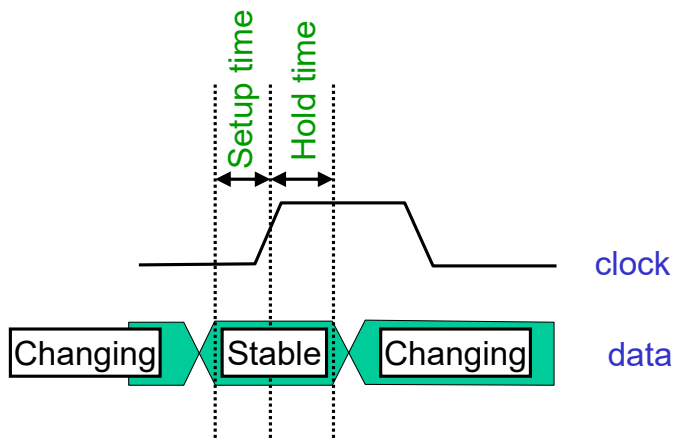- *Setup time*: time before clock edge during which data input must be stable.
- *Hold time*: time after clock event for which data input must remain stable.




CLOCK SKEW (1)

 - Clock must arrive at all memory elements in time to load data.
- The maximum difference between clock arrival times is the *clock skew*.



CLOCK SKEW (2)

 - Clock skew values larger than the flip-flop input-output delay lead to malfunctioning: some computations will be based on the next state rather than the current state.




Is this a hold-time or a setup-time violation?

What can we do about it?

CLOCK DISTRIBUTION

- Goals:
 - deliver clock to all memory elements with acceptable skew;
 - deliver clock edges with acceptable sharpness.
- Clocking network design is one of the greatest challenges in the design of a large chip.

H-TREE

 

CLOCK TREE

- In order to balance the delay from the clock source to the flip-flops, *clock trees* are used.
- They use optimal buffer sizing principles.
- In current-day practice clock trees are generated during layout as wiring delay is significant.

